


1.1. $C_0 = 200 \text{ pF}$
 $C = 300 \text{ pF}$ pour $H_R = 1$
 $C = C_0 (1 + \alpha H_R)$

$$\beta = 1 + \alpha H_R$$

$$\alpha = \frac{C}{C_{0H_R}} - \frac{1}{H_R} = \frac{1}{H_R} \left(\frac{C}{C_0} - 1 \right)$$

$$\alpha = \frac{300}{200} - 1 = \frac{3}{2} - 1 = 1,5 - 1 = 0,5$$

1.2.

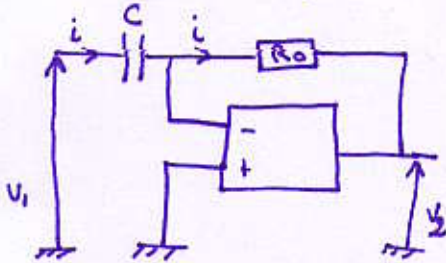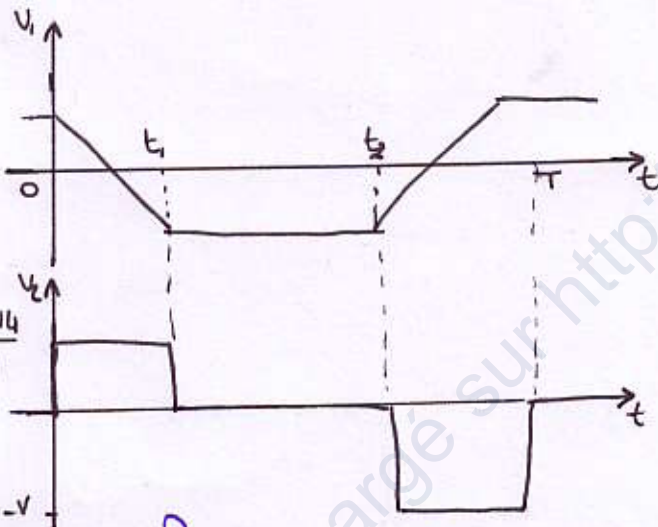

$$\dot{z}^+ = \dot{z}^- = 0 \text{ is ideal}$$

$V^+ = V^- = 0V$ ACP lineaire

$$v_2 = -R\omega i \text{ or } i = \frac{dq}{dt} = C \frac{dV_C}{dt} = C \frac{dV_1}{dt}$$


donc $y_2 = -R_0 C \frac{dw_1}{dt}$

1.3.




$$V = +R_C \frac{2 \times 14}{t_1} = 2.48V$$

1.4

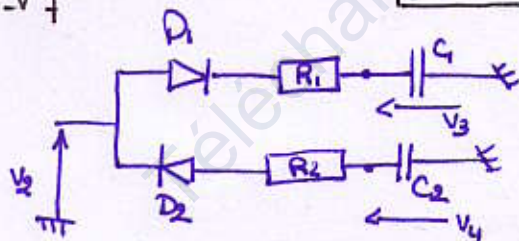


① V_1 est passante pour $V_2 > 0$

② D_2 $V_2 < 0$

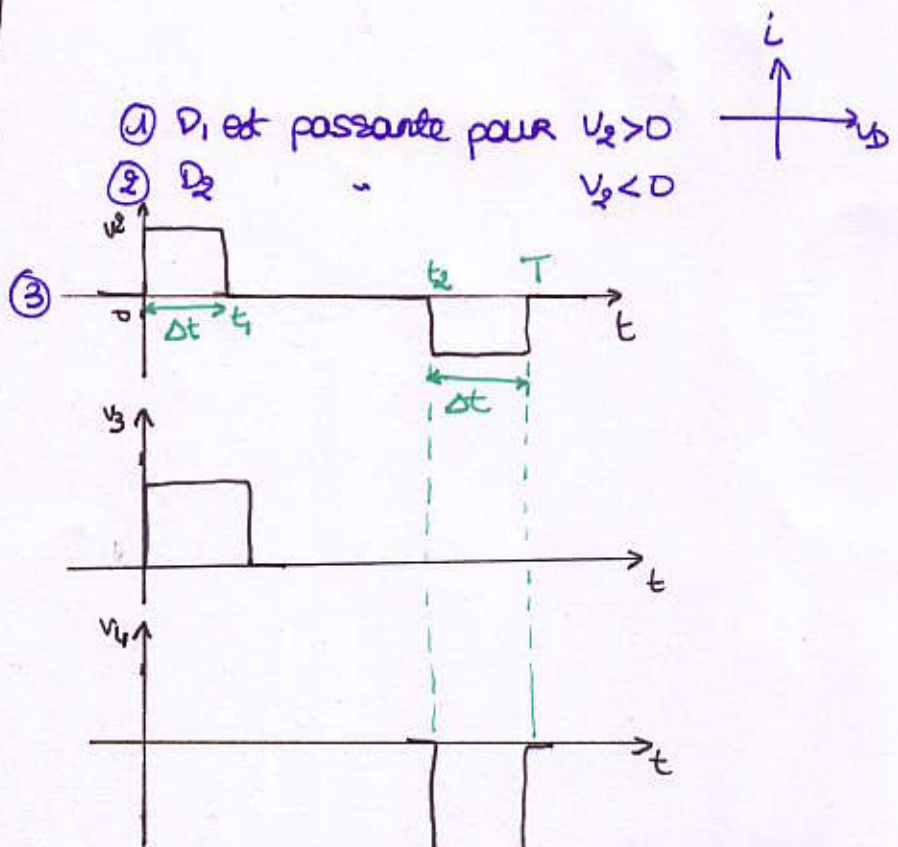


R est très petit, la charge et la décharge sont quasi instantanées

2.1. $V^+ = V^- = V_4$

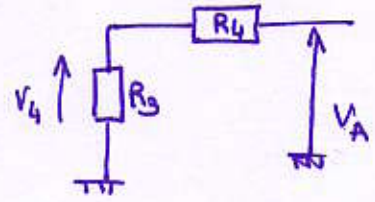

$$V_4 = \frac{R_3}{R_3 + R_4} V_A$$

2.2.

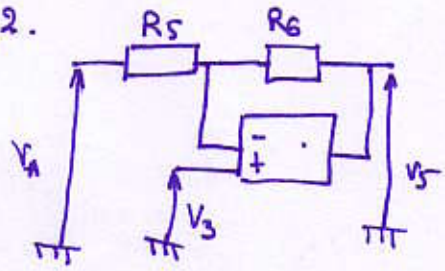

$$V^+ = V^- = V_3$$

$$V_3 = \frac{R_5 V_5 + R_6 V_A}{R_5 + R_6}$$

$$R_5 V_5 = V_3 (R_5 + R_6) - R_6 V_A$$

$$V_5 = \frac{R_5 + R_6}{R_5} V_3 - \frac{R_6}{R_5} V_A$$

2.3.

$$V_5 = \left(\frac{R_5}{R_5} + \frac{R_6}{R_5} \right) V_3 - \frac{R_6}{R_5} \left(1 + \frac{R_4}{R_3} \right) V_4$$

$$V_5 = \left(1 + \frac{R_6}{R_5} \right) V_3 - \frac{R_6}{R_5} \left(1 + \frac{R_4}{R_3} \right) V_4$$

2.4.

$$V_5 = A_D (V_3 - V_4) + A_{nc} (V_3 + V_4) / 2$$

2.4.1.

si $V_3 = V_4$

$$V_5 = \frac{A_{nc}}{2} (V_3 + V_4) = A_{nc} V_4$$

$$V_5 = A_{nc} V_3$$

$$V_5 = \left[1 + \frac{R_6}{R_5} - \frac{R_6}{R_5} \left(1 + \frac{R_4}{R_3} \right) \right] V_3$$

donc $A_{nc} = 1 - \frac{R_6}{R_5} \times \frac{R_4}{R_3}$

2.4.2.

si $V_3 = -V_4$

$$V_5 = 2 A_D V_3$$

$$V_5 = \left[1 + \frac{R_6}{R_5} + \frac{R_6}{R_5} \left(1 + \frac{R_4}{R_3} \right) \right] V_3$$

donc $2 A_D = 1 + \frac{2 R_6}{R_5} + \frac{R_6 R_4}{R_5 R_3}$

2.5.

$$A_{nc} = 1 - \frac{R_6 R_4}{R_5 R_3} = 0 \Rightarrow \frac{R_6 R_4}{R_5 R_3} = 1$$

Soit $R_6 R_4 = R_5 R_3$. Soit $A_D = \frac{1}{2} \left(2 + \frac{2 R_6}{R_5} \right) = 1 + \frac{R_6}{R_5}$

2.6.

$$R_5 = R_4 = 20 \text{ k}\Omega = R$$

$$\begin{cases} R_6 R_4 = R_5 R_3 \\ 1 + \frac{R_6}{R_5} = 1,5 \end{cases} \Rightarrow \begin{cases} R_6 = R_3 \\ 1 + \frac{R_6}{R_5} = 1,5 \end{cases}$$


$$\frac{R_6}{R_5} = 0,5 \Rightarrow R_6 = R_5 \times 0,5 = 10 \text{ k}\Omega$$

Donc $R_5 = R_4 = 20 \text{ k}\Omega$

$R_6 = R_3 = 10 \text{ k}\Omega$

2.7

3

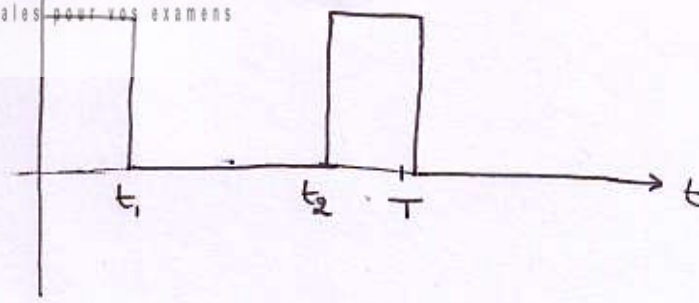

III. Choix d'un CAN

3.1. $v_s = 5,54 (1 + 0,5 H_R)$


$0 < H_R < 1$.

$5,54 < 5,54 (1 + 0,5 H_R) < 8,31$.

3.2. $\Delta v_s = \frac{\partial v_s}{\partial H_R} \Delta H_R$.

$\Delta v_s = 0,5 \times 5,54 \Delta H_R = 2,77 \Delta H_R$ si $\Delta H_R = 0,005$

$\Delta v_s = 0,01385 V$.

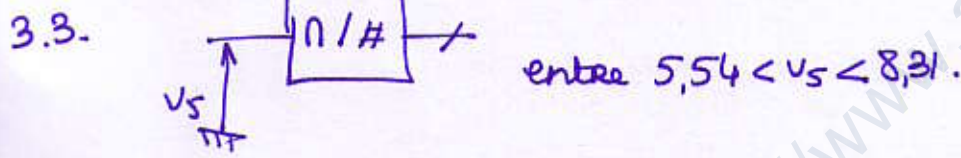

On veut un $q = 0,0138$ or $q = \frac{v_{max}}{nd \text{ (bit)}}$
($5^{\text{th}} = 0,005 = \Delta H_R$)

si $N_{bit} = 8 \Rightarrow 255$

$N_{bit} = 12 \Rightarrow 4095$

ici $v_{max} = 10$.

$q_1 = \frac{10}{255} = 0,03922 > q$

$q_2 = \frac{10}{4095} = 0,00244 < q$ donc ok

CAN4