

TPIL - Corrigé Sujet Elect 2005

①

1 >

1.1 > $I = \frac{10^{-5}}{\sqrt{2}} = 0,707 \text{ mA}$ (0,5)

1.2.1 > $|i| < I_c \Rightarrow R_2 = 0 \Rightarrow V_2 = 0 \text{ V}$ (0,5)



1.2.2 > $|i| > I_c \Rightarrow R_2 = 1 \text{ k}\Omega$
 $\Rightarrow V_2 = R_2 \cdot i$ (10,5)

1.2.3 > $V_{Lc} = R_L \cdot I_c = 0,5 \text{ V}$ (0,5)

1.2.4 > $I_{R_{eq}} = 1 \text{ mA} > I_c$
 donc $V_2(t) = R_2 \cdot I_{R_{eq}} = 1 \text{ V}$ (10,5)

1.3 > (1)
 1.4 >

q. d. $|i(t)| < I_c$ cad q. d. $V_2 < 0,5 \text{ V}$
 alors $V_2 = 0 \text{ V}$.

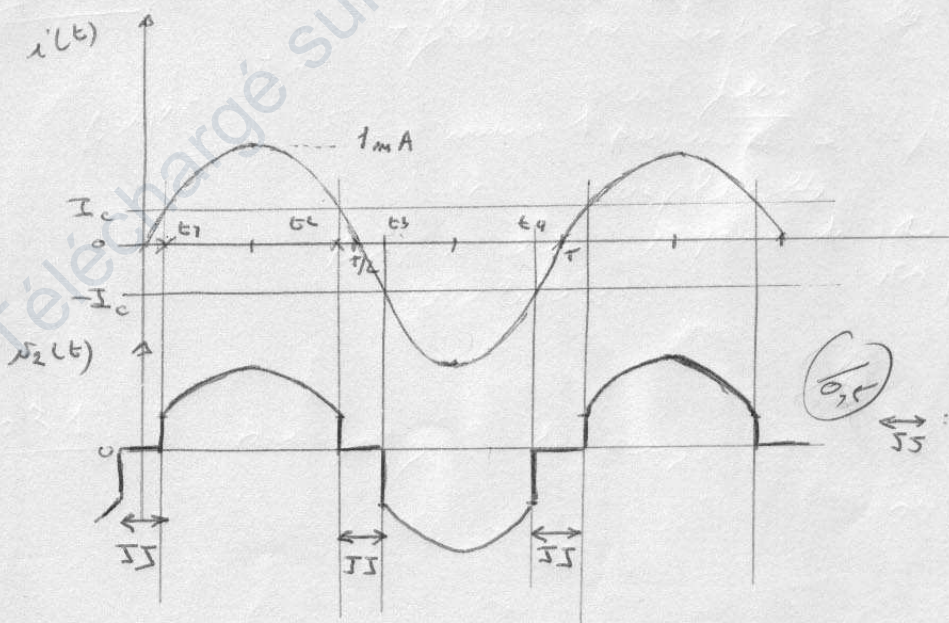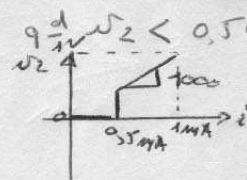

(0,5)
 SS : intervalle
 durant lequel
 SS est
 supraconducteur

1.5) $i(t) = I_c = I_{R_{eq}} \sin(\omega t_1)$ (2)
 $\Rightarrow \omega t_1 = \text{Arccsin} \left(\frac{I_c}{I_{R_{eq}}} \right) \Rightarrow \left[t_1 = \frac{1}{\omega} \text{Arccsin} \left(\frac{I_c}{I_{R_{eq}}} \right) \right]$ (1)


1.6) $t_1 = 167 \mu s$ (0.5)

2) 2.1) Comp 1 : pas de réaction $\left\{ \begin{matrix} > 0 \\ < 0 \end{matrix} \right\} \Rightarrow$ AOP en saturation
 $\Rightarrow V_3 = V_{sat} \text{ ou } 0V \Rightarrow V_3 = 5V \text{ ou } 0V$


$\begin{cases} V^- = 0V \\ V^+ = V_1 \end{cases} \Rightarrow E = V_1$ (1)

$V_3 = 5V \text{ si } E > 0 \Rightarrow \text{si } V_1 > 0$
 $V_3 = 0V \text{ si } E < 0 \Rightarrow \text{si } V_1 < 0$

2.2)

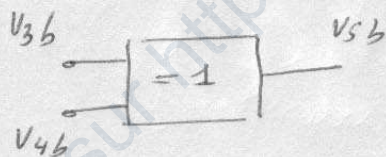

V_{3b}	V_{4b}	V_{5b}
0	0	0
0	1	1
1	0	1
1	1	0

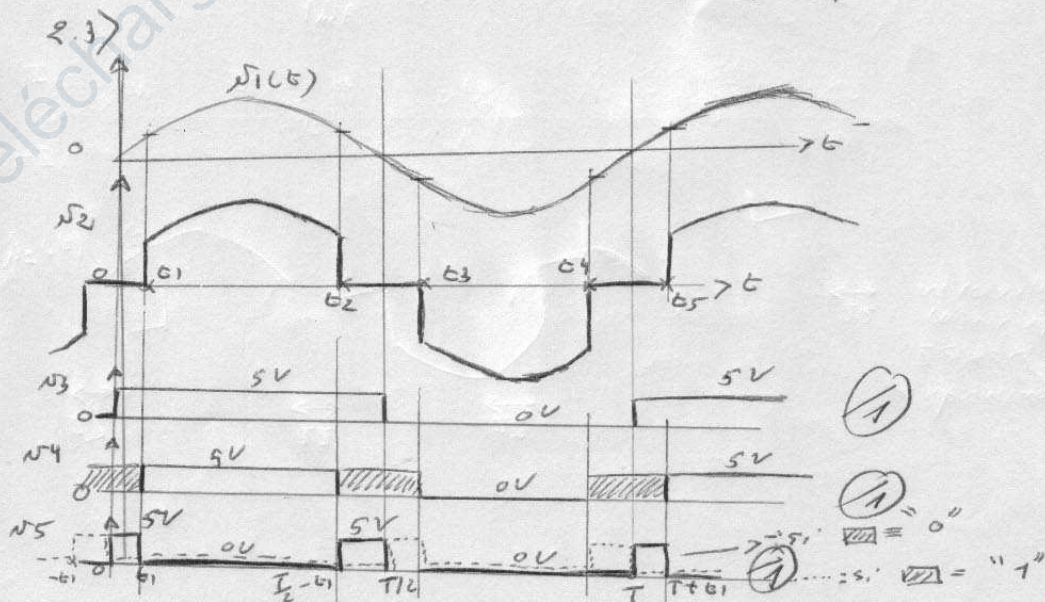(1)


$$2.4 \rangle \langle v_s \rangle = \frac{1}{T} \times (5 \times t_1 + 5 \times \frac{1}{2} \times \frac{1}{T} \times t_1) = \frac{1}{T} \times 10 t_1 \quad (3)$$

$$\langle v_s \rangle = \frac{10 t_1}{T} = 10 f \cdot t_1 \quad (1)$$

3 >

$$3.1 \rangle \underline{Z}_{eq} = \underline{Z}_{R4} // \underline{Z}_C = \frac{R_4}{j \cdot \omega C} = \frac{R_4}{1 + j R_4 \omega C} \quad (0.5)$$

3.2 > Montage inverseur :

$$\underline{T} = \frac{v_6}{v_5} = - \frac{\underline{Z}_{eq}}{\underline{Z}_{R3}} = - \frac{R_4}{R_3} \times \left(\frac{1}{1 + j R_4 \omega C} \right) \quad (1)$$

3.3 >

$$|\underline{T}| = \frac{R_4}{R_3} \times \frac{1}{\sqrt{1 + (R_4 \omega C)^2}} \quad (1)$$

$$G_{dB} = 20 \log \frac{R_4}{R_3} - 10 \log [1 + (R_4 \omega C)^2] \quad (0.5)$$

3.4 > Parce bas actif 1^{er} ordre. (1)

$$3.5 \rangle \underline{T}_{max} = \frac{R_4}{R_3} \Rightarrow G_{max} = 20 \log \left(\frac{R_4}{R_3} \right) \quad (1)$$

$$3.6 \rangle \underline{T} = \frac{\underline{T}_0}{1 + j \frac{\omega}{\omega_c}} \Rightarrow \underline{T}_0 = \frac{R_4}{R_3} \quad (1)$$

$$3.7 \rangle R_4 = \frac{1}{2 \pi f_c C} = 159.155 \Omega \quad (0.5)$$

$$G_{max} = 2 = 20 \log \left(\frac{R_4}{R_3} \right) \Rightarrow \frac{2}{20} = \log \left(\frac{R_4}{R_3} \right)$$

$$\Rightarrow \frac{|Z_{20}|}{10} = \frac{R_4}{R_3} \Rightarrow R_4 = 1,26 R_3$$

$$\Rightarrow \underline{R_3 = 126421 \Omega} \quad (0,5)$$

$$3.8) \quad |T|_{\omega=100\text{Hz}} = \frac{R_4}{R_3} \times \frac{1}{\sqrt{1 + \left(\frac{100}{10}\right)^2}} = 0,12527 \quad (0,5)$$

$$\Rightarrow \underline{G_{dB} = 20 \log |T| = -18 \text{ dB}} \quad (0,5)$$

